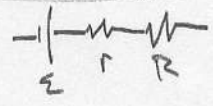
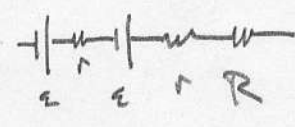





19.47 | The only way for the current to be less than double is if one of the batteries has internal resi. We can calculate this (assume  $\mathcal{E} = 1.5V$ )

single:   $I_1 = \frac{\mathcal{E}}{r+R}$

double:   $I_2 = \frac{2\mathcal{E}}{2r+R}$

With  $I_1 = .2A$ ,  $I_2 = .33A$ ,  $\mathcal{E} = 1.5V$  gives  $R = 5.9\Omega$ ,  $r = 1.6\Omega$

19.52 |

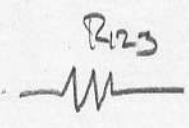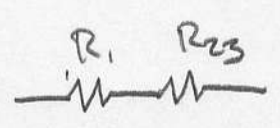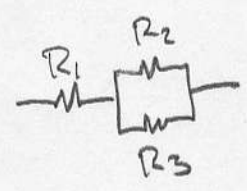

$$R_{23} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$


$$= \frac{1}{\frac{1}{5} + \frac{1}{20}}$$

$$= 4\Omega$$

$$R_{123} = R_1 + R_{23}$$

$$= 14\Omega$$


19.66 |

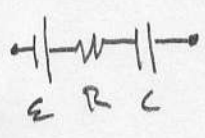a]   $\mathcal{E} - IR - Q/C = 0$  when fully charged  $I \rightarrow 0$

$$|Q_{max}| = \mathcal{E}C$$

b] Placing a dielectric of strength  $K$  changes  $C$  as the material inside becomes polarized leading to a greater potential.

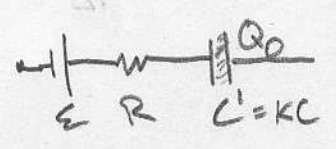c]  $C' = KC$  hence  $Q'_{max} = K\mathcal{E}C$  and  $I'$  can be found by




$$\mathcal{E} - IR - Q_0/C' = 0$$

$$I = \frac{Q_0/KC + \mathcal{E}}{R}$$


let  $Q_0 \equiv Q_{max}$  before the dielectric

19.67

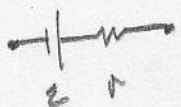
a]   $\epsilon - Ir = 0$   
 $r = \frac{\epsilon}{I} = \frac{9}{18} = \frac{1}{2} \Omega$

b]  $P = I\Delta V = (18)(9) = 162 \text{ W}$

c]  $P = I\Delta V = I^2 r = (18)^2 \cdot \frac{1}{2} = 162 \text{ W}$   
 $P\Delta t = E = (162)(15) = 162 \text{ J}$

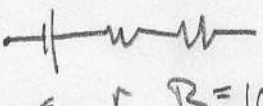d]   $R = 10$   
 $I = \frac{\epsilon}{r+R} = \frac{9}{\frac{1}{2}+10} = \frac{9}{12} = \frac{3}{4} \text{ A}$

$P_R = I^2 R = (\frac{3}{4})^2 \cdot 10 = 7.5 \text{ W}$

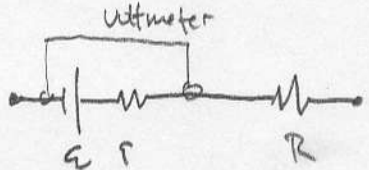f]   $\Delta V = \epsilon - Ir = 9 - \frac{3}{4} \cdot \frac{1}{2} = 9 - \frac{3}{8} = 8.625 \text{ V}$

19.71

node:

$$I_2 + I_1 - I_3 - I_4 = 0$$

$$I_4 + I_5 - I_1 = 0$$

loop:

$$-I_2 R_2 - I_4 R_4 + I_5 R_5 + \mathcal{E}_2 = 0$$

$$\mathcal{E} - I R_1 - I_3 R_3 - I_5 R_5 = 0$$

$$I_4 R_4 - I_3 R_3 - I_5 R_5 = 0$$


$\Delta V_{D \rightarrow A}$  can take any path! I took  $D \rightarrow E \rightarrow F \rightarrow G \rightarrow H \rightarrow A$

$$\Delta V_{D \rightarrow A} = -[-\mathcal{E}_2 - I_5 R_5] \text{ another path DCHA gives}$$


$$= -[-I_2 R_2 - I_4 R_4]$$

$$P_2 = I_2 \Delta V = I_2 \mathcal{E}_2$$

19.73

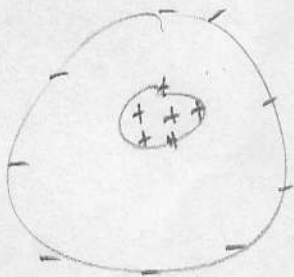

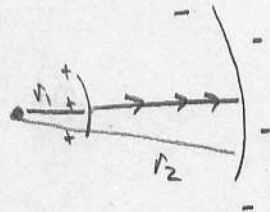Replace inner shell by point charge (spherical conductor!)



Integrate along path shown

$$\Delta V = -\int \vec{E} \cdot d\vec{l}$$

$$\vec{E} = \vec{E}_{\text{inner}} + \vec{E}_{\text{outer}} \text{ inside conductor}$$

$$= \frac{kQ}{r^2} \hat{r}$$

$$\Delta V = -\int_{r_1}^{r_2} \frac{kQ}{r^2} dr = -kQ \left( \frac{-1}{r} \right) \Big|_{r_1}^{r_2} = kQ \left( \frac{1}{r_2} - \frac{1}{r_1} \right)$$

$$C = Q/\Delta V = (Q[1/r_2 - 1/r_1])^{-1}$$

part b comes from the Taylor expansion of  $\frac{1}{1+s} = \frac{1}{1+s/r_2} \approx \frac{1}{r_2} (1 - s/r_2 + \dots)$