


Name: _____

Answer the questions in the spaces provided on the question sheets. If you run out of room for an answer, continue on the back of the page.

- If electrons are flowing towards the right of a segment of a wire, then the current is flowing towards
 - the right.
 - the left.**
 - neither left nor right.
- What is the charge on a wire that has a cross-section area of 0.00004m^3 with electrons drifting along with a drift velocity $v_d = 0.0156\text{m/s}$ and the density of the charges in the wire is $5.3 \times 10^{24}/\text{m}^3$. The charge of the electrons is, -1.602×10^{-19} C. What is the current?

Solution:

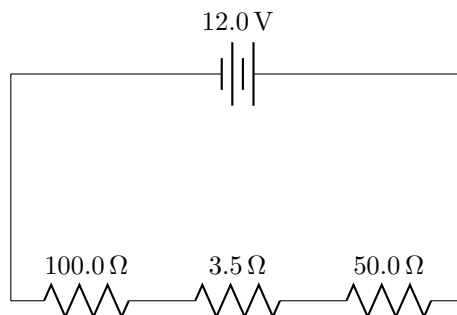
$$I = (5.3 \times 10^{24}/\text{m}^3) (-1.602 \times 10^{-19}\text{C})(0.0156\text{m/s})(0.00004\text{m}^2) = -5.30 \times 10^{-1}\text{A}$$



- What is the equivalent resistance and current in the circuit shown above?


Solution: Since the resistors are in series, the equivalent resistance is the sum of the resistors:
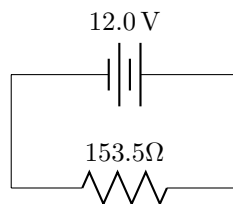
$$R_{eq} = 3.5\Omega + 100.0\Omega + 50.0\Omega = 153.5\Omega$$



The current in the circuit is the same as the current in the equivalent circuit since there is only one loop:
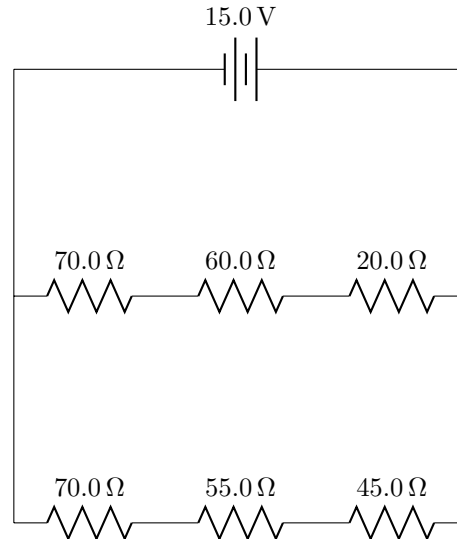
$$I = \frac{V}{R_{eq}} = \frac{12.0\text{V}}{153.5\Omega} = 0.08\text{A}$$




4. Find the equivalent resistor in the above circuit and the current in each branch of the circuit. *Hint: first treat each branch individually in series and find the equivalent resistor for each branch, then treat the parallel problem.*

Solution: First find the equivalent circuit in each branch in series. The top branch gives

$$R_{eqT} = 60.0\Omega + 70.0\Omega + 20.0\Omega = 150.0\Omega$$

and the bottom branch gives,
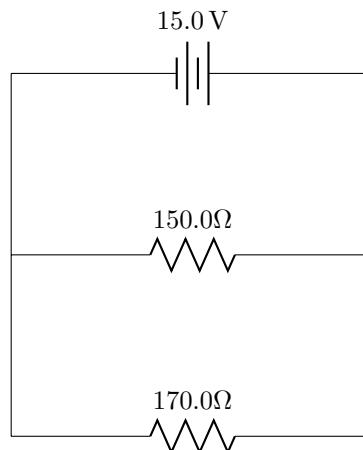
$$R_{eqB} = 55.0\Omega + 70.0\Omega + 45.0\Omega = 170.0\Omega$$



The current passing through the top equivalent resistor is:


$$I_T = \frac{V}{R_{eqT}} = \frac{15.0V}{150.0\Omega} = 0.10A$$

and through the bottom resistor:

$$I_B = \frac{V}{R_{eqB}} = \frac{15.0V}{170.0\Omega} = 0.09A$$

Now that we have reduced this to the simplest possible parallel circuit, we find the final equivalent resistor for parallel resistors:

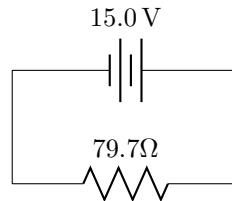
$$\frac{1}{R_{eq}} = \frac{1}{R_T} + \frac{1}{R_B} = \frac{1}{150.0\Omega} + \frac{1}{170.0\Omega}$$
$$R_{eq} = 79.7\Omega$$



So now we can solve for the current **that passes through the battery branch**:


$$I = \frac{V}{R_{eq}} = \frac{15.0\text{V}}{79.7\Omega} = 0.19\text{A}$$

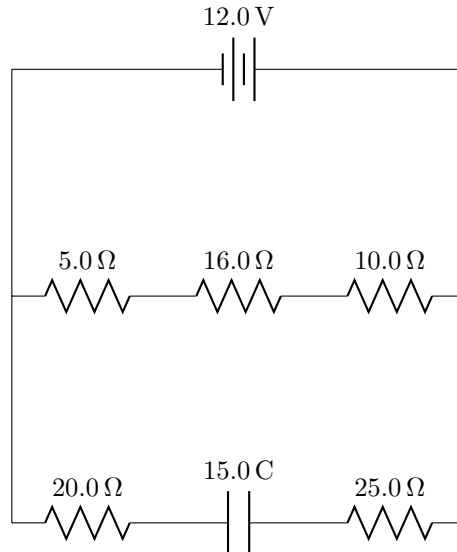We see that $I = I_T + I_B$ as required by the **junction rule**.



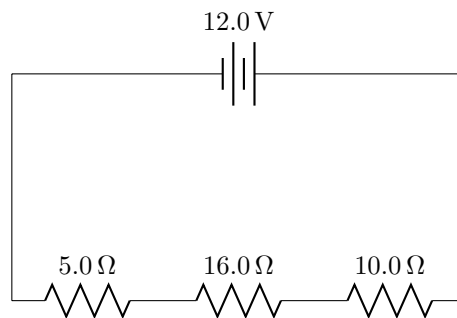
5. When a circuit with a capacitor in it is first turned on, current flows as if there were no capacitor. After a very long period of time, the capacitor becomes fully charged and no current flows through the branch that has a capacitor on it. Using this knowledge, find the equivalent resistor for the entire circuit at time $t = 0$ when the circuit is first activated and at a long long time later. Find the current in each branch in both cases.

Solution: Let's first take the case when the circuit has been open for a very long period of time:



Since the resistors are in series, the equivalent resistance is the sum of the resistors:

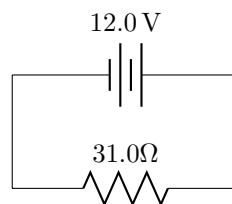
$$R_{eq} = 16.0\Omega + 5.0\Omega + 10.0\Omega = 31.0\Omega$$



The current in the circuit is the same as the current in the equivalent circuit since there is only one loop:

$$I = \frac{V}{R_{eq}} = \frac{12.0\text{V}}{31.0\Omega} = 0.39\text{A}$$

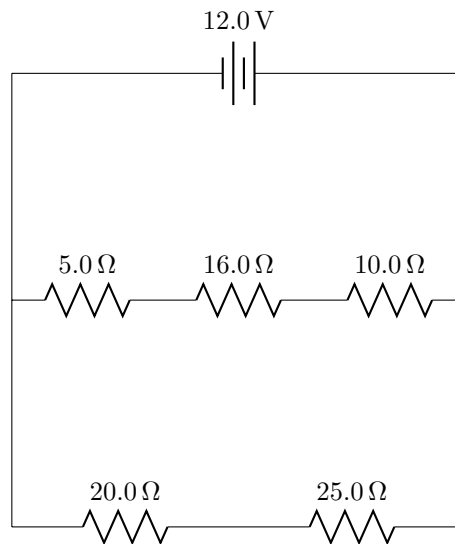Second case: Now suppose that the circuit was just opened, in which case the capacitor acts as if it were just a wire (in only that initial instance of time is that true):




First find the equivalent circuit in each branch in series. The top branch gives

$$R_{eqT} = 16.0\Omega + 5.0\Omega + 10.0\Omega = 31.0\Omega$$

and the bottom branch gives,
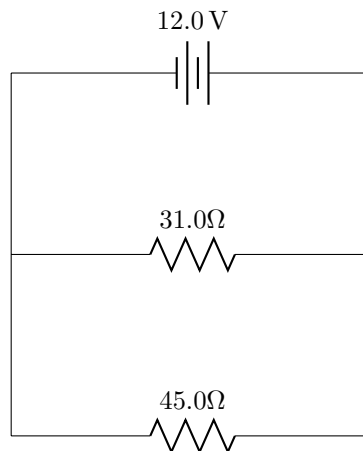
$$R_{eqB} = 20.0\Omega + 25.0\Omega = 45.0\Omega$$



The current passing through the top equivalent resistor is:


$$I_T = \frac{V}{R_{eqT}} = \frac{12.0\text{V}}{31.0\Omega} = 0.39\text{A}$$

and through the bottom resistor:

$$I_B = \frac{V}{R_{eqB}} = \frac{12.0\text{V}}{45.0\Omega} = 0.27\text{A}$$

Now that we have reduced this to the simplest possible parallel circuit, we find the final equivalent resistor for parallel resistors:

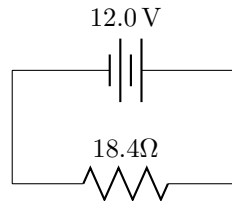
$$\frac{1}{R_{eq}} = \frac{1}{R_T} + \frac{1}{R_B} = \frac{1}{31.0\Omega} + \frac{1}{45.0\Omega}$$
$$R_{eq} = 18.4\Omega$$



So now we can solve for the current **that passes through the battery branch**:


$$I = \frac{V}{R_{eq}} = \frac{12.0\text{V}}{18.4\Omega} = 0.65\text{A}$$

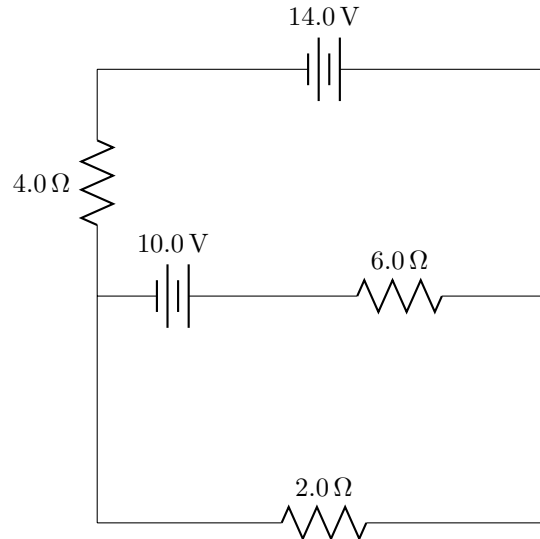We see that $I = I_T + I_B$ as required by the **junction rule**.



6. Using the loop and junction rules, find the current in each branch of the above circuit. Label each branch and give its current.

Solution:

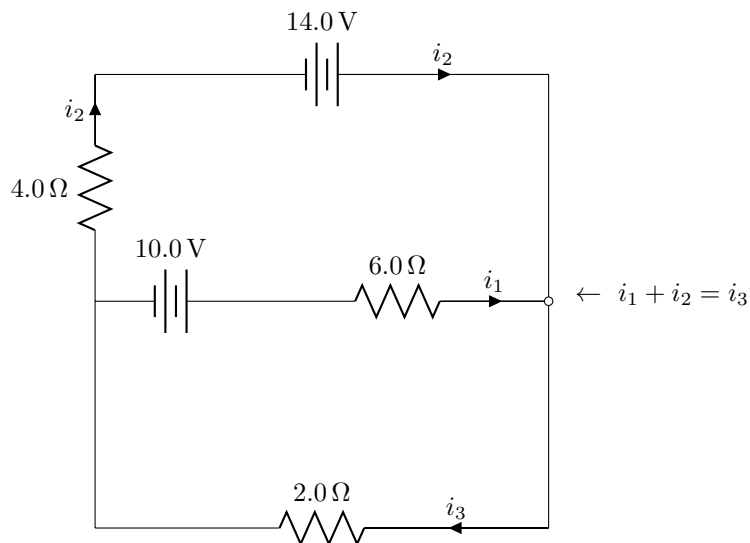

Our first equation is acquired from applying the junction rule at the node indicated in the figure, which gives us that $i_1 + i_2 = i_3$. We require two more equations to have three total independent equations to solve for the three unknown variables. Having two loops, we apply the loop rule for each:

$$0 = 14.0\text{V} + i_1 6.0\Omega - 10.0\text{V} - i_2 4.0\Omega \rightarrow i_2 = 1.0\text{A} + i_1 1.5$$

$$0 = 10.0\text{V} - i_1 6.0\Omega - i_3 2.0\Omega \rightarrow i_3 = 5.0\text{A} - 3.0i_1$$

Our first equation from the junction rule becomes:

$$i_1 + 1.0A + i_1 1.5 = 5.0A - 3.0i_1$$

Or,

$$i_1 = 0.7A$$

Then,

$$i_3 = 2.8A$$

$$i_2 = 2.1A$$

As a final check, we see that this conforms to the requirement that $i_1 + i_2 = i_3$.