

# Recitation 6

## Chapter 21

**Problem 35.** Determine the current in each branch of the circuit shown in Figure P21.35.

Let  $I_1$  be the current on the left branch (going down),  $I_2$  be the current on the middle branch (going up), and  $I_3$  be the current on the right branch (going up). From Kirchoff's junction rule, we know.

$$I_1 = I_2 + I_3 \quad (1)$$

Let  $\epsilon_2 = 4.00 \text{ V}$  be the voltage across the middle battery, and  $\epsilon_3 = 12.0 \text{ V}$  be the voltage across the right battery. Using our knowledge of parallel resistors, we find

$$R_1 = 8.00\Omega \quad (2)$$

$$R_2 = 5.00\Omega + 1.00\Omega = 6.00\Omega \quad (3)$$

$$R_3 = 3.00\Omega + 1.00\Omega = 4.00\Omega \quad (4)$$

We can use Ohm's law to find the voltage drops across them in the direction of their current.

Now using Kirchoff's loop rule on the left-center and left-right loops respectively we have

$$0 = \epsilon_2 - I_2 R_2 - I_1 R_1 \quad (5)$$

$$0 = \epsilon_3 - I_3 R_3 - I_1 R_1 \quad (6)$$

So we have our three equations relating our unknown currents. If you're comfortable with linear algebra, you can express these as a matrix

$$\begin{pmatrix} 0 \\ \epsilon_2 \\ \epsilon_3 \end{pmatrix} = \begin{pmatrix} -1 & 1 & 1 \\ R_1 & R_2 & 0 \\ R_1 & 0 & R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} \quad (7)$$

Inverting the 3x3 matrix, we get

$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} -0.2308 & 0.0385 & 0.0577 \\ 0.3077 & 0.1154 & -0.0769 \\ 0.4615 & -0.0769 & 0.1346 \end{pmatrix}^{-1} \begin{pmatrix} 0 \\ 4.00 \\ 12.0 \end{pmatrix} = \begin{pmatrix} 0.8462 \\ -0.4615 \\ 1.3077 \end{pmatrix} \text{ A} \quad (8)$$

Where  $I_2 < 0$  indicates that current actually flows in the opposite direction to what we expected.

If you're not comfortable with linear algebra, you can solve the equations using your method of choice. If no methods make sense to you, come talk to me or get someone else to teach you one.

**Problem 38.** The following equations describe an electric circuit:

$$-(220\Omega)I_1 + 5.80 \text{ V} - (370\Omega)I_2 = 0 \quad (9)$$

$$(370\Omega)I_2 + (150\Omega)I_3 - 3.10 \text{ V} = 0 \quad (10)$$

$$I_1 + I_3 - I_2 = 0 \quad (11)$$

(a) Draw a diagram of the circuit. (b) Calculate the unknowns and identify the physical meaning of each unknown.

(b) Solve using your method of choice. With linear algebra:

$$\begin{pmatrix} 5.80 \text{ V} \\ 3.10 \text{ V} \\ 0 \end{pmatrix} = \begin{pmatrix} 220\Omega & 370\Omega & 0 \\ 0 & 370\Omega & 150\Omega \\ 1 & -1 & 1 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} \quad (12)$$

Inverting the 3x3 matrix, we get

$$\begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0.0031 & -0.0022 & 0.3267 \\ 0.0009 & 0.0013 & -0.1942 \\ -0.0022 & 0.0035 & 0.4791 \end{pmatrix}^{-1} \begin{pmatrix} 5.80 \text{ V} \\ 3.10 \text{ V} \\ 0 \end{pmatrix} = \begin{pmatrix} 11.0 \\ 9.13 \\ -1.87 \end{pmatrix} \text{ mA} \quad (13)$$

**Problem 42.** A  $C = 2.00 \text{ nF}$  capacitor with an initial charge of  $Q = 5.10 \mu\text{C}$  is discharged through an  $R = 1.30\Omega$  resistor. (a) Calculate the current in the resistor  $t_a = 9.00 \mu\text{s}$  after the resistor is connected across the terminals of the capacitor. (b) What charge remains on the capacitor after  $t_b = 8.00 \mu\text{s}$ ? (c) What is the maximum current in the resistor?

(a) The current through the entire circuit follows

$$I = \frac{Q}{RC} e^{-t/RC} \quad (14)$$

So

$$I(t_a) = \frac{5.10 \cdot 10^{-6} \text{ C}}{1.30\Omega \cdot 2.00 \cdot 10^{-6} \text{ F}} e^{\frac{-9.00 \cdot 10^{-6} \text{ s}}{1.30\Omega \cdot 2.00 \cdot 10^{-6} \text{ F}}} = 61.6 \text{ mA} \quad (15)$$

(b) The charge on the capacitor follows

$$q = Q e^{-t/RC} \quad (16)$$

So

$$I(t_a) = 5.10 \cdot 10^{-6} \text{ C} e^{\frac{-8.00 \cdot 10^{-6} \text{ s}}{1.30\Omega \cdot 2.00 \cdot 10^{-6} \text{ F}}} = 235 \mu\text{C} \quad (17)$$

(c) Plugging  $t = 0$  into our equation from (a) we have

$$I_{max} = \frac{Q}{RC} = 1.96 \text{ A} \quad (18)$$

**Problem 45.** The circuit in Figure P21.45 has been connected for a long time. (a) What is the voltage  $V_c$  across the capacitor? (b) If the battery is disconnected, how long does it take the capacitor to discharge to  $V'_c = 1/10 \cdot V$ ?

Labeling the resistors counterclockwise from the upper left we have  $R_1 = 1.00\Omega$ ,  $R_2 = 4.00\Omega$ ,  $R_3 = 2.00\Omega$ , and  $R_4 = 8.00\Omega$ . Let  $V = 10.0 \text{ V}$  be the voltage on the battery and  $C = 1.00 \mu\text{F}$  be the capacitance of the capacitor.

(a) Because the system has been running for a long time, the system must be close to equilibrium. Therefore, the current through the capacitor must be zero (otherwise the voltage across the capacitor would be changing, and you wouldn't be at equilibrium). The resistor bridge then reduces to two parallel circuits, and we can apply Ohm's law to determine  $V_c$ .

Starting with the left side of the bridge (calling the current  $I_L$ ),

$$V = I_L(R_1 + R_2) \quad (19)$$

$$I_L = \frac{V}{R_1 + R_2} \quad (20)$$

And on the right calling the current  $I_R$

$$I_R = \frac{V}{R_3 + R_4} \quad (21)$$

So using Ohm's law to compute the voltage across the capacitor, we call the voltage on the bottom wire 0 and have the voltage  $V_L$  on the left at

$$V_L = I_L R_2 = \frac{V R_2}{R_1 + R_2} = 8 \text{ V} \quad (22)$$

And the voltage  $V_R$  to the right of the capacitor is

$$V_R = I_R R_3 = \frac{V R_3}{R_3 + R_4} = 2 \text{ V} \quad (23)$$

So the voltage across the capacitor is

$$V_c = V_L - V_R = 6 \text{ V} \quad (24)$$

(b) Once we remove the battery, we see that the capacitor discharges through two paths in parallel,  $R_1 \rightarrow R_4$  and  $R_2 \rightarrow R_3$ . The equivalent resistances of these two parallel branches (top and bottom) are

$$R_T = R_1 + R_4 \quad (25)$$

$$R_B = R_2 + R_3 \quad (26)$$

So the total equivalent resistance is

$$R = \left( \frac{1}{R_T} + \frac{1}{R_B} \right)^{-1} = 3.60\Omega \quad (27)$$

The voltage of a discharging capacitor depends on time according to

$$V'_c = V_c e^{-t/RC} \quad (28)$$

So using  $V'_c = V_c/10$  we have

$$10 = \frac{V_c}{V'_c} = \frac{V_c}{V_c e^{-t/RC}} = e^{t/RC} \quad (29)$$

$$\ln(10) = \frac{t}{RC} \quad (30)$$

$$t = RC \ln(10) = 8.29 \mu\text{s} \quad (31)$$

**Problem 53.** An electric heater is rated at  $P_H = 1500$  W, a toaster at  $P_T = 750$  W, and an electric grill at  $P_G = 1000$  W. The three appliances are connected to a common  $V = 120$  V household circuit. (a) How much current does each draw? (b) Is a circuit with a  $V_{max} = 25.0$  A circuit breaker sufficient in this situation? Explain your answer.

(a) Using  $P = IV$  we have

$$I_H = \frac{P_H}{V} = 12.5 \text{ A} \quad (32)$$

$$I_T = \frac{P_T}{V} = 6.25 \text{ A} \quad (33)$$

$$I_G = \frac{P_G}{V} = 8.33 \text{ A} \quad (34)$$

$$(35)$$

(b) If all the appliances are running together, the circuit draws

$$I = I_H + I_T + I_G = 27.1 \text{ A} \quad (36)$$

So you will be fine with a 25 A breaker unless you plan to run all three at the same time.

**Problem 58.** A battery with emf  $\epsilon$  is used to charge a capacitor  $C$  through a resistor  $R$  as shown in Figure 21.25. Show that half the energy supplied by the battery appears as internal energy in the resistor and that half is stored in the capacitor.

The total current through the system is given by

$$I = I_0 e^{-t/RC} = \frac{\epsilon}{R} e^{-t/RC} \quad (37)$$

Which allows us to compute the energy put out by the battery. Power is the time derivative of energy so

$$E_b = \int_0^{\infty} P \cdot dt \quad (38)$$

$$= \int_0^{\infty} I\epsilon \cdot dt \quad (39)$$

$$= \frac{\epsilon^2}{R} \int_0^{\infty} e^{-t/RC} \cdot dt \quad (40)$$

$$= \frac{\epsilon^2}{R} \left. -RCe^{-t/RC} \right|_0^{\infty} \quad (41)$$

$$= \frac{\epsilon^2}{R} (0 - (-RCe^0)) \quad (42)$$

$$= C\epsilon^2 \quad (43)$$

Similarly for the energy absorbed by the resistor

$$E_r = \int_0^{\infty} P \cdot dt \quad (44)$$

$$= \int_0^{\infty} I^2 R \epsilon \cdot dt \quad (45)$$

$$= \frac{\epsilon^2}{R} \int_0^{\infty} e^{-2t/RC} \cdot dt \quad (46)$$

$$= \frac{\epsilon^2}{R} \left. \frac{-RC}{2} e^{-2t/RC} \right|_0^{\infty} \quad (47)$$

$$= \frac{E_b}{2} = \frac{1}{2} C\epsilon^2 \quad (48)$$

And we already know the energy stored in a capacitor with a voltage  $\epsilon$  is

$$E_c = \frac{1}{2} C\epsilon^2 = \frac{E_b}{2} \quad (49)$$

So the battery energy splits evenly between the capacitor and the resistor, and we're done.