

## Homework 6

### Chapter 21

**Problem 40.** A dead battery is charged by connecting it to the live battery of another car with jumper cables (Fig. P21.40). Determine the current in the starter and in the dead battery.

**Problem 46.** A  $C = 10.0 \mu\text{F}$  capacitor is charged by a  $\epsilon = 10.0 \text{ V}$  battery through a resistance  $R$ . The capacitor reaches a potential difference of  $V_C(t_f) = 4.00 \text{ V}$  at the instant  $t_f = 3.00 \text{ s}$  after the charging begins. Find  $R$ .

**Problem 55.** Four  $V = 1.50 \text{ V}$  AA batteries in series are used to power a transistor radio. If the batteries can move a charge of  $\Delta Q = 240 \text{ C}$ , how long will they last if the radio has a resistance of  $R = 200\Omega$ ?