## **Physics 115:** Contemporary Physics III

Spring 2013 Programming Assignment 2

Due May 3, 2013

## **Resistive and Capacitive Circuits**

 Solve the complex resistive circuit shown in Figure 20.46 (Section 20.10, p. 819) of Chabay & Sherwood. Use the following numerical values for the components:

$$\begin{array}{ll} {\rm emf}_1 = 6V, & r_1 = 0.5\Omega \\ {\rm emf}_2 = 9V, & r_2 = 0.25\Omega \\ R_1 = 1\Omega, & R_2 = 2\Omega, & R_3 = 2\Omega \\ R_5 = 10\Omega, & R_6 = 3\Omega \\ \end{array} \begin{array}{ll} R_7 = 6\Omega \end{array}$$

Following the text, identify the unknown currents in the problem and write down, using the Kirchhoff Node and Loop rules, a sufficient number of equations to solve for these currents. Solve these equations numerically using the solve function in the numpy.linalg package. Verify that the currents you obtain do indeed satisfy the equations you derived.

2. Solve numerically the discharging capacitor problem. In the RC circuit shown in Chabay & Sherwood Figure 20.39 (p. 813), write

$$RI + \frac{Q}{C} = 0,$$

with I = dQ/dt, so

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

(the same differential equation as for the current in a charging capacitor!). Set RC = 1 (that is, take RC as the unit of time), so

$$\frac{dQ}{dt} + Q = 0,$$

and imagine that the capacitor discharges not continuously, but in small steps, each of time duration  $\Delta t$ . Then in time  $\Delta t$ , we have

$$\frac{\Delta Q}{\Delta t} = -Q,$$

so the change in the capacitor charge is

$$\Delta Q = -Q\Delta t.$$

Starting from an initial charge  $Q_0 = Q(0) = 1$ , and taking steps  $\Delta t = 0.01$ , calculate approximately how the charge on the capacitor changes in time, for  $t = 0, \Delta t, 2\Delta t, ..., 10$ , using the rule

$$Q(t + \Delta t) = Q(t) - Q(t)\Delta t$$

Compare your solution with the analytic solution to the differential equation

$$Q = Q_0 e^{-t/RC} \ (= e^{-t} \ \text{here})$$

by plotting them on the same graph.